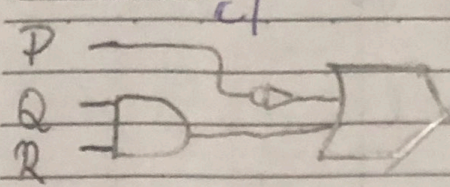


...



g^0	a	$\bar{C}\bar{D}$	$\bar{C}D$	CD	$C\bar{D}$
$\bar{A}\bar{B}$					
$\bar{A}B$	1	1			
$A\bar{B}$	1	1			
AB					


$B\bar{C}$

l	$\bar{C}\bar{D}$	$\bar{C}D$	CD	$C\bar{D}$
$\bar{A}\bar{B}$				
$\bar{A}B$		1		
$A\bar{B}$		1		
AB				1

$B\bar{C}D + AB\bar{C}D$

16	$\bar{C}\bar{D}$	$\bar{C}D$	CD	$C\bar{D}$	$AB + B\bar{C}D + A\bar{D} + AC$
$\bar{A}\bar{B}$	0	0	0	0	
$\bar{A}B$	0	0	1	0	
$A\bar{B}$	1	1	1	1	
AB	0	1	1	1	

17	$\bar{C}\bar{D}$	$\bar{C}D$	CD	$C\bar{D}$	$A\bar{C} + \bar{C}\bar{D} + AB + B\bar{C} + A\bar{D}$
$\bar{A}\bar{B}$	1	0	0	0	
$\bar{A}B$	1	1	0	0	
$A\bar{B}$	1	1	1	1	
AB	1	1	0	1	

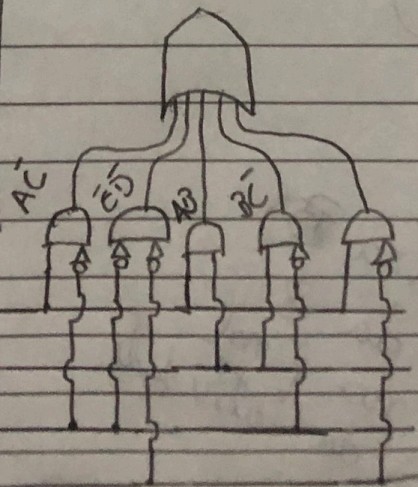

Circuito:

25 30 35 40


23 = 1000

A	B	C	D	S
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	1
0	1	1	1	1
1	0	0	0	0
1	0	0	1	0
1	0	1	0	1
1	0	1	1	1
1	1	0	0	0
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1


Mapas

	$\bar{C}\bar{D}$	$\bar{C}D$	CD	$C\bar{D}$
$A\bar{B}$	0	0	0	0
$\bar{A}B$	0	0	1	1
AB	0	1	1	1
$A\bar{B}$	0	0	1	1

AC + BC + ABD

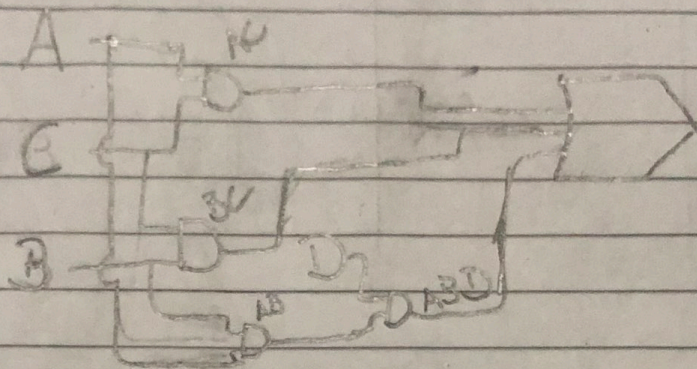

24°	$\bar{C}$	C	$AC + BC + AB$
$\bar{A}\bar{B}$	0	0	
$\bar{A}B$	0	1	
$A\bar{B}$	1	1	
AB	0	1	

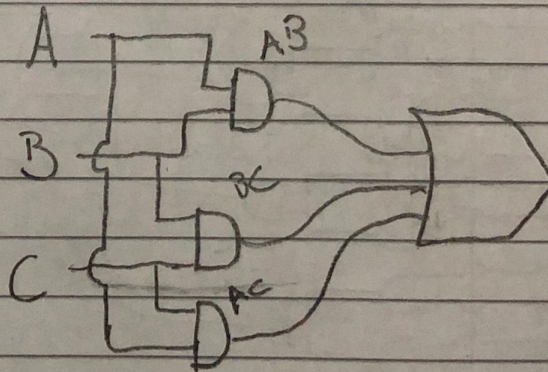

26° A	$\bar{C}\bar{D}$	$\bar{C}D$	CD	$C\bar{D}$	$S_1 = \bar{B}C\bar{D} + \bar{A}B\bar{C}\bar{D} + \bar{A}\bar{B}C\bar{D} + \bar{A}BCD +$
$\bar{A}B$	0	1	0	(1)	$AB\bar{C}\bar{D}$
$\bar{A}B$	1	0	1	0	
$A\bar{B}$	0	1	0	0	
$A\bar{B}$	0	0	0	(1)	

S2 do outro lado

...

	$\bar{C}\bar{D}$	$\bar{C}D$	$C\bar{D}$	CD	$\bar{C}\bar{D} + \bar{A}\bar{C} + \bar{A}\bar{D} + \bar{A}\bar{B}C + \bar{A}\bar{B}D$
$\bar{A}\bar{B}$	1	0	0	0	
$\bar{A}B$	1	0	0	1	
$A\bar{B}$	1	1	0	0	
AB	1	1	1	0	

$\bar{A}\bar{B}$	$\bar{C}$	C	$S_1 = \bar{A}\bar{B} + AC$	S_2	$\bar{C}$	C	$\bar{A}\bar{C} + \bar{B}\bar{C} + \bar{A}\bar{B}C$
$\bar{A}\bar{B}$	1	1		$\bar{A}\bar{B}$	1	0	
$\bar{A}B$	0	0		$\bar{A}B$	1	0	
$A\bar{B}$	0	1		$A\bar{B}$	1	0	
AB	0	1		AB	0	1	

$S = 1$

$$S = ABCD + \bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}B\bar{C}D + A\bar{B}C\bar{D}$$

